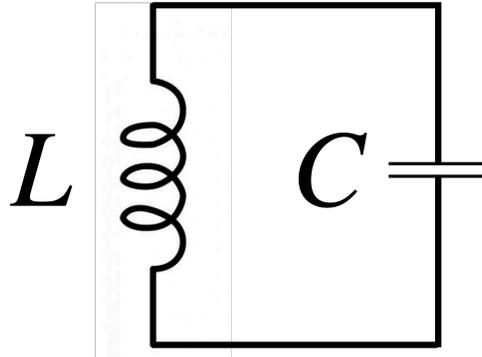


PHYS2063 Wave Physics Homework #1 Due Thursday 25 Aug 2022

This homework assignment is due at the start of class on the date shown. You may submit a PDF of your solutions to the Canvas page for the course, or bring a paper copy to class.

This diagram shows an inductor L and a capacitor C connected in series:



The voltage drop across an inductor is $V_L = LdI/dt$ where I is the current flowing through the inductor. The voltage drop across a capacitor is $V_C = q/C$ where q is the charge on the capacitor plates. Kirchoff's voltage law says that the sum of all voltage drops around a closed loop is zero. You can assume that the wires connecting the inductor and capacitor have no resistance. The charge (and current) are functions of time t .

Find the differential equation for the charge $q(t)$ and show that it implies that $q(t)$ has a simple harmonic time dependence. Find the (angular) frequency ω in terms of L and C for these oscillations.

Assume the values $L = 0.1$ mH and $C = 1$ μ F. At time $t = 0$ the current in the circuit is $I_0 = 100$ μ A and the charge on the capacitor is $q_0 = 1$ nC. Find the amplitude and phase of the oscillations for $q(t)$.